

Assignment 2



Name: Nafinur LEO

ID: 20-92195-1

Subject Name: Electronic Devices

Section: J

1. The voltage of GaAs is 1.2V

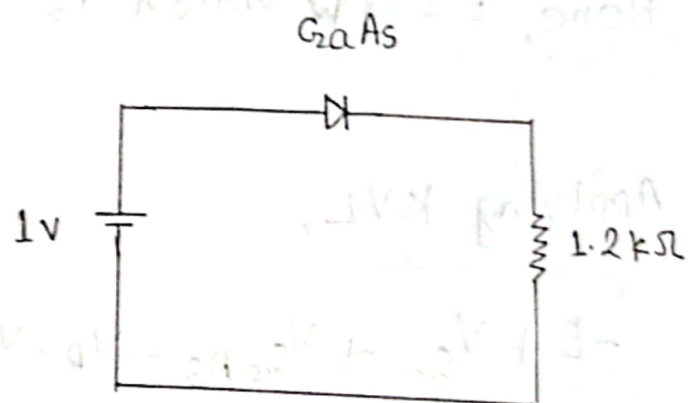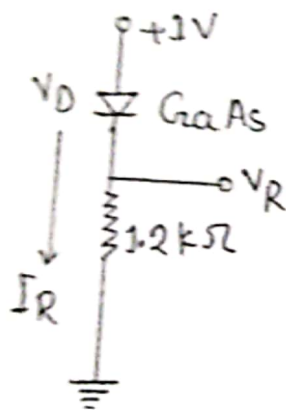


Here, we give less voltage than the knee voltage of GaAs. So, the circuit will close.

Given that,  $V_D = 1\text{V}$

$$I_R = I_D = 0$$

$$\therefore V_R = 0 \text{ (Ans.)}$$

2.

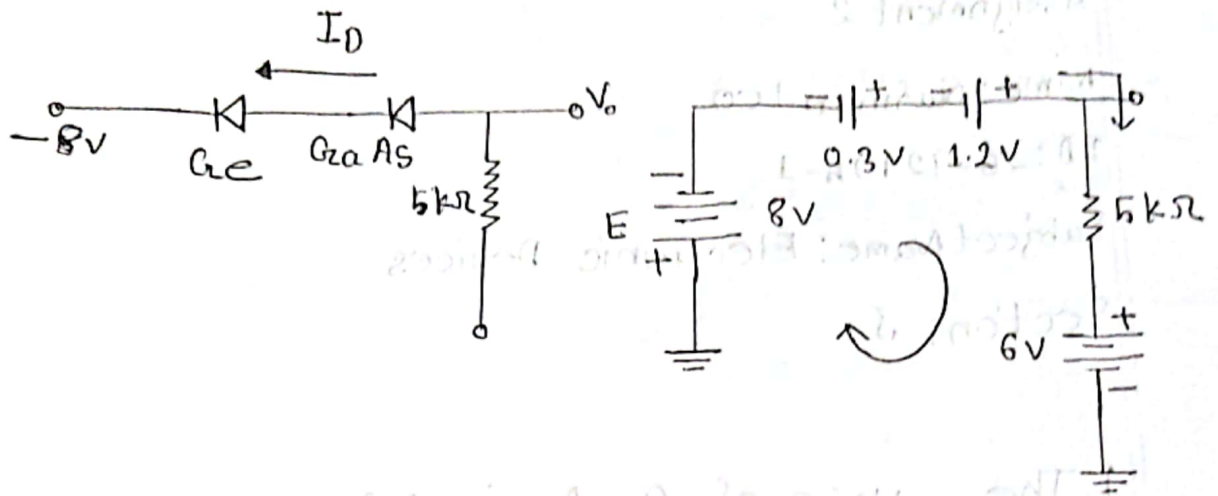

Here,  $E = 8V$  which is greater than  $(0.3 + 1.2)V = 1.5V$

Applying KVL,

$$-E + V_{Gc} + V_{GaAs} - V_R - V_o = 0$$

$$\Rightarrow -8 + 0.3 + 1.2 - 6 - V_o = 0$$



$$\Rightarrow V_o = -12.5 V$$

$$\therefore I_D = \frac{V_o}{R} = \frac{-12.5}{5}$$

$$= -2.5 A \quad (\text{Ans:})$$

Sub:

3.

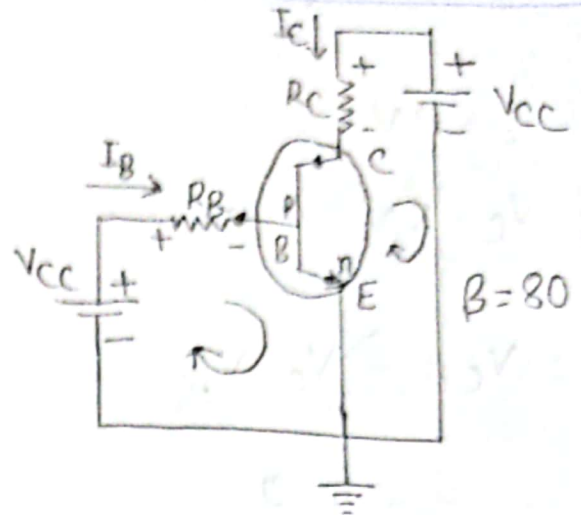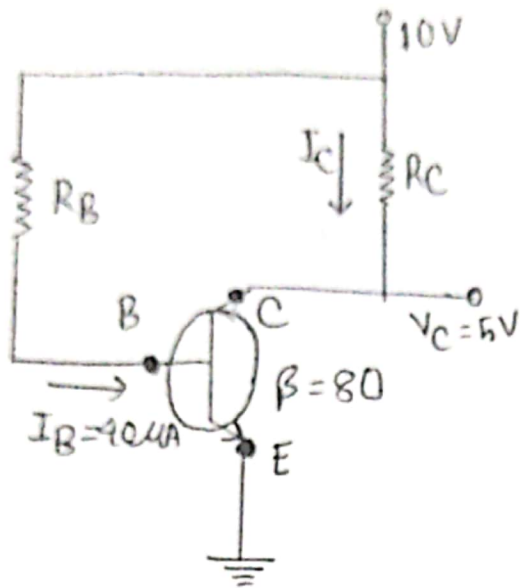

Here,  $I_C = \beta I_B$

$$= 80 \times 40 \times 10^{-6}$$

$$= 3.2 \times 10^{-3} \text{ A}$$

$$= 3.2 \text{ mA}$$

Applying KVL,

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

$$= \frac{10 - 0.7}{40 \times 10^{-6}}$$

$$= 232.5 \text{ k}\Omega$$

Sub: \_\_\_\_\_

Page: \_\_\_\_\_  
Time: \_\_\_\_\_ Date: \_\_\_\_/\_\_\_\_/\_\_\_\_

$$V_E = 0V$$

$$V_C = 5V$$

$$\therefore V_{CE} = V_C - V_E$$

$$= 5 - 0$$

$$= 5V$$

Applying KVL,

$$+V_{CE} + I_C \times R_C - V_{CC} = 0$$

$$\Rightarrow R_C = \frac{V_{CC} - V_{CE}}{I_C}$$

$$= \frac{10 - 5}{3.2 \times 10^{-3}}$$

$$= 1.5625k\Omega$$

(Ans:)

Sub: \_\_\_\_\_

Day: \_\_\_\_\_

Time: \_\_\_\_\_

Date: / /

4. i)

→  
Negative Half cycle

→  
Positive Half Cycle


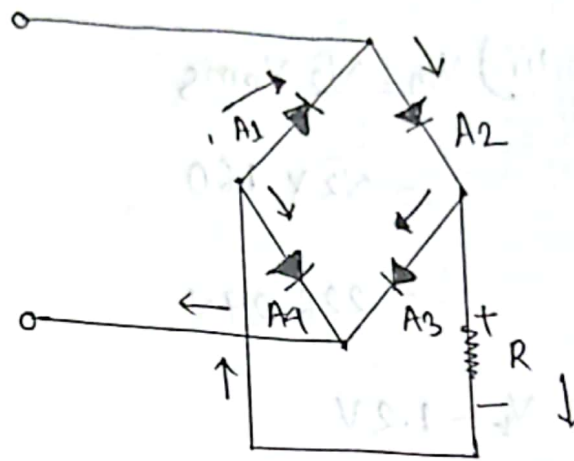


Figure: Full Wave Bridge Rectifier Circuit

$$\begin{aligned} \text{ii) } V_m &= \sqrt{2} V_{rms} \\ &= \sqrt{2} \times 160 \\ &= 226.27 \text{ V} \end{aligned}$$

Here,

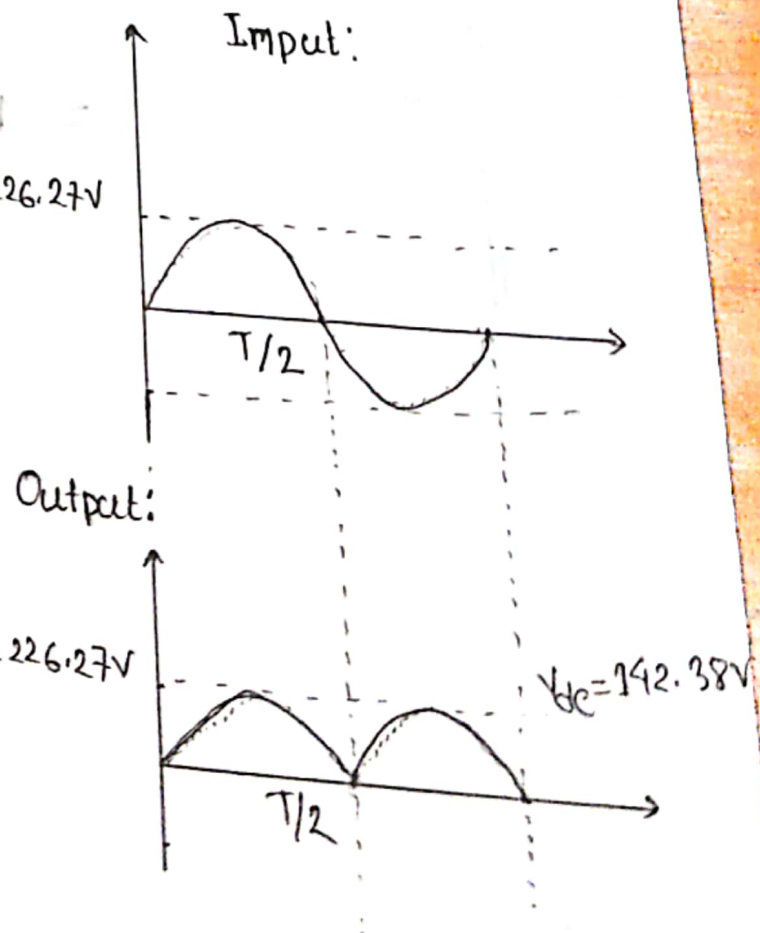
$$\begin{aligned} V_{dc} &= 0.636 \times (V_m - 2V_k) \\ &= 0.636 \times (226.27 - 2 \times 1.2) \\ &= 142.38 \text{ V} \end{aligned}$$





$$\begin{aligned} \text{iii) } V_m &= \sqrt{2} V_{rms} \\ &= \sqrt{2} \times 160 \\ &= 226.27 \text{ V} \end{aligned}$$

$$V_k = 1.2 \text{ V}$$

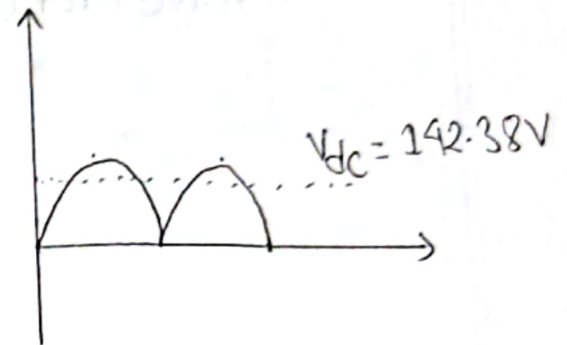

$$\text{Output Voltage } V_{dc} = 0.636 \times (V_m - 2V_k)$$

$$= 0.636 \times (226.27 - 2 \times 1.2)$$

$$= 142.38 \text{ V}$$

(Ans.)